## 3 Resistor Network Cheat Sheet

Design:

To map voltage  $[V_{\rm IL}:V_{\rm IH}]$  into voltage  $[V_{\rm OL}:V_{\rm OH}]$  :

Voltage gain 
$$A = \frac{V_{IH} - V_{IL}}{V_{IH} - V_{IL}}$$

Choose input resistor  $R_1$ 

Find Thévenin equivalent voltage of remaining two resistors:

$$V_{\mathrm{Th}} = \frac{V_{\mathrm{OL}} - AV_{\mathrm{IL}}}{1 - A}$$

Find Thévenin equivalent resistance of remaining two resistors

$$R_2 || R_3 = \frac{AR_1}{1 - A}$$

Find divider ratio of remaining two resistors:

$$B = \frac{V_{\mathrm{Th}} - V_{ee}}{V_{cc} - V_{ee}}$$

Find remaining two resistors:

$$R_2 = \frac{R_{\text{Th}}}{B}$$
 ;  $R_3 = \frac{R_{\text{Th}}}{1 - B}$ 

Analysis:

Output resistance:

$$R_{\text{out}} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$$

Open-circuit output voltage:

$$V_{\text{out}} = \frac{\frac{V_{\text{in}}}{R_1} + \frac{V_{\text{cc}}}{R_2} + \frac{V_{\text{ee}}}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

