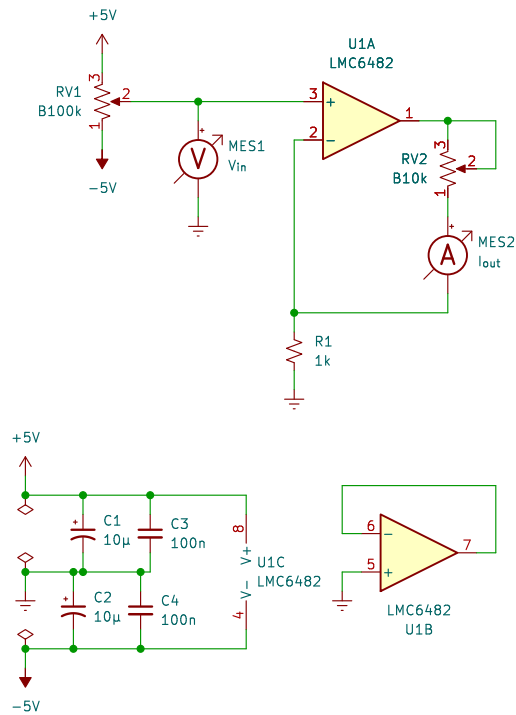



### Example 1: Floating Load



$I_{out} = V_{in}/R_1$

- Observe that small output currents are constant as load varies.
- Observe that power supply + R1 limit compliance.
- Observe that output current is NOT returned to ground.

### Example 2: Load returned to ground

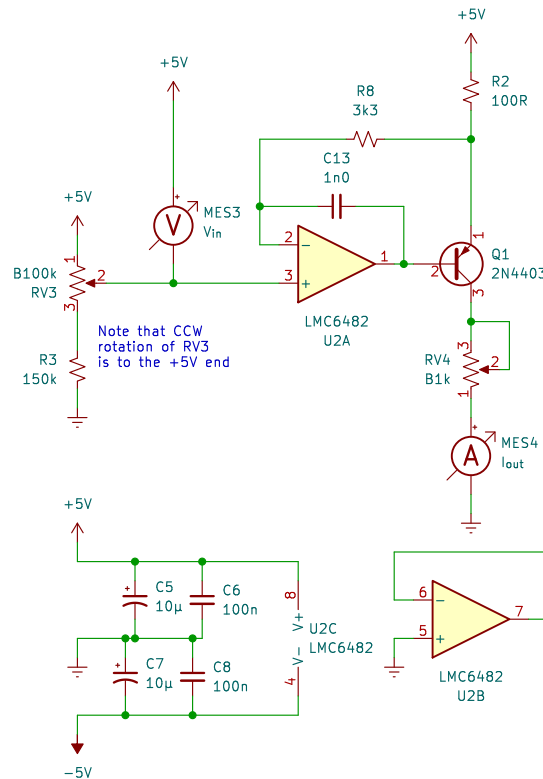


$I_{out} \approx (V_{cc} - V_{in})/R_2$

- Observe handling of larger load currents.
- Observe that power supply + R2 still limit compliance.
- Note base current error
- Mention Early effect
- Replace Q1 with BS250P MOSFET - same pinout:
  - Base current error goes away
  - No Early effect
  - Feedback network may be needed to prevent oscillation.
- Add R8, C13 if needed. (R8=0 otherwise)

Limited to 20 mA because pot has only 1/20W power dissipation  
Driving the input could be a problem. RRIO is only nearly so.
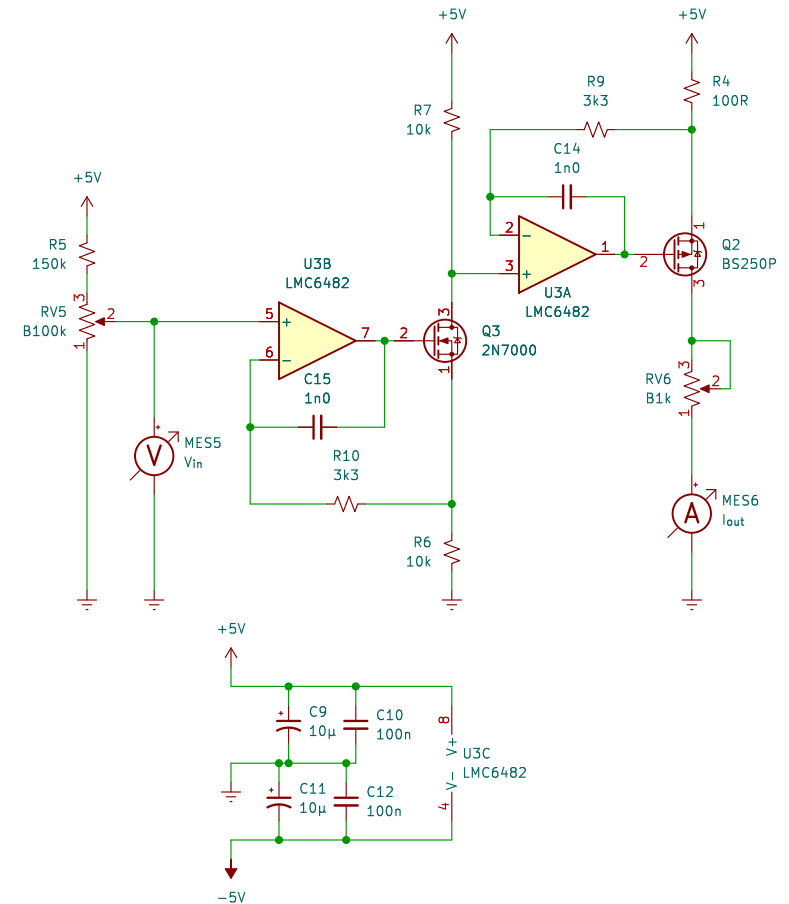
### Example 3: Load and source both referenced to ground



$I_{out} = V_{in} R_7/R_6 R_4$

- Now  $V_{in}$  has a sensible range.
- Still only single ended.



Op-Amp Basics  
Episode 14 - Transconductance Amplifiers 1  
**Kluidges from Kevin's Cave**

Sheet: /  
File: Transconductance1.kicad\_sch

**Title: Transconductance Amplifier Examples, part 1**

Size: A Date: 2026-02-16  
KiCad E.D.A. kicad 7.0.11+dfsg-1build4

Rev: E  
Id: 1/1