



Connect voltmeters to base and collector of Q1.

Vary RV1 and observe output voltage as a function of input voltage.

Observe the linearity of the relation.

Calculate voltage gain and offset, verify against model prediction.