



Connect function generator to J1, set to a sine wave of about 0.5 Vpp.

AC couple an oscilloscope to J2, observe that the circuit amplifies with a gain of about -10 and an offset of about 19 V.

Increase input level and observe clipping from both saturation and cutoff.