
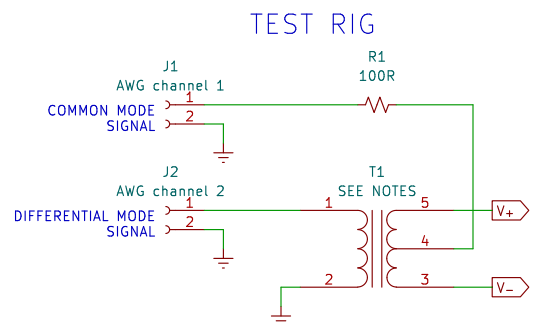


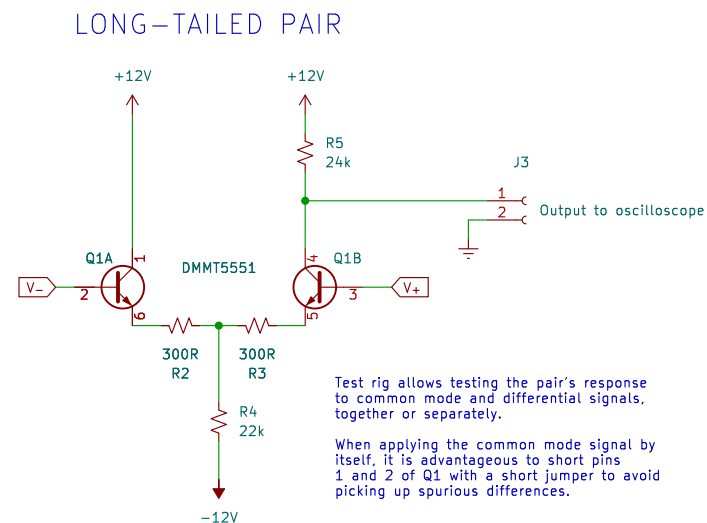


T1 is a small 120V:6.3VCT power transformer Triad Magnetics F-14X or similar. Suitable transformers can often be scavenged from discarded equipment with linear power supplies.




Test rig allows testing the pair's response to common mode and differential signals, together or separately.

When applying the common mode signal by itself, it is advantageous to short pins 1 and 2 of Q1 with a short jumper to avoid picking up spurious differences.

POWER AND BYPASSING

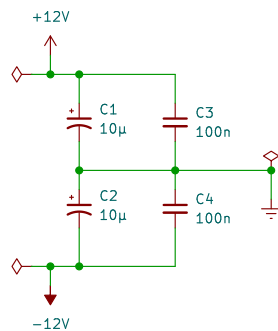

Place C3, C4 as close to Q1 as possible.

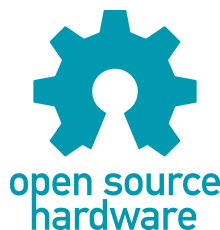

Transistors 101, episode 14

The differential pair: the heart of analog circuits

Kludges from Kevin's Cave

Sheet: /

File: LongTailedPair.kicad_sch

Title: Long-tailed pair: the basic circuit

Size: USLetter Date: 2026-05-13

KiCad E.D.A. kicad 7.0.11+dfsg-1build4

Rev: B

Id: 1/1